

THE TECHNICAL UNIVERSITY OF KOŠICE
FACULTY OF ELECTRICAL ENGINEERING AND INFORMATICS
DEPARTMENT OF ELECTRONICS AND MULTIMEDIA COMMUNICATIONS

Basic of electronics
Measurement no.3
Half- wave rectifier


Ac. Year: 2010/2011
Class / Group: 1.st / A1
Study : Applied Informatics



Tasks:

- 1.) Measure the static transfer characteristic of half- wave rectifier
- 2.) Measure the output waveform of half- wave rectifier in time domain with (and without) capacitor C, for different parameters of input periodic signal (frequency)

Circuit diagram:

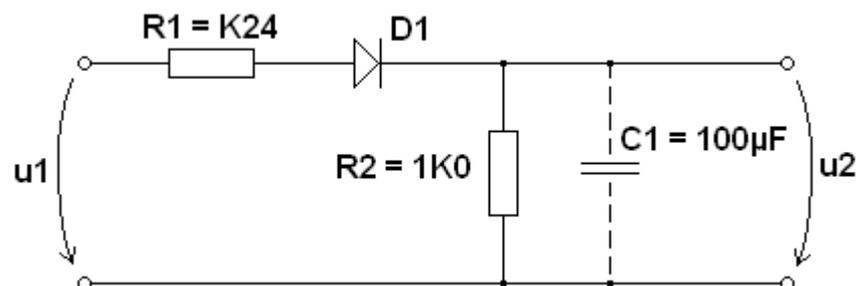


Theory:

General rectifier:


Rectifier is used to modify AC to DC. It is the most common connection using diodes. A rectifier is an electrical device that converts alternating current (AC), which periodically reverses direction, to direct current (DC), which is in only one direction, a process known as rectification. Rectifiers have many uses including as components of power supplies and as detectors of radio signals. Rectifiers may be made of solid state diodes, vacuum tube diodes, mercury arc valves, and other components.

Half-wave rectifier:

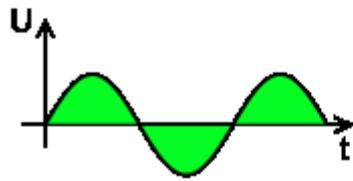
In half wave rectification, either the positive or negative half of the AC wave is passed, while the other half is blocked. Because only one half of the input waveform reaches the output, it is very inefficient if used for power transfer. Half-wave rectification can be achieved with a single diode in a one-phase supply, or with three diodes in a three-phase supply.



Input voltage

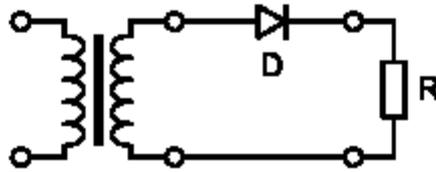

Half-wave rectifier

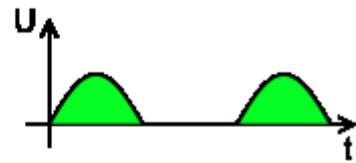


Output voltage

The output DC voltage of a half wave rectifier can be calculated with the following two ideal equations:

$$V_{dc} = \frac{V_{peak}}{\pi}$$

$$V_{rms} = \frac{V_{peak}}{2}$$

Equations

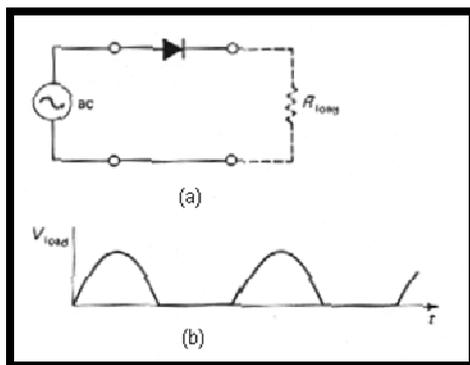


Half-wave rectifier with a diode (a). Input voltage sine wave (ac) with an amplitude much larger than $\sim 0.6 V$ U_{DF} after passing through a silicon diode will have on the output of the form (b).


Only one half-cycle sinusoidal input voltage is used for rectify- from there the name Half-wave rectifier.

Full-wave rectifier:


A full-wave rectifier converts the whole of the input waveform to one of constant polarity (positive or negative) at its output. Full-wave rectification converts both polarities of the input waveform to DC and is more efficient. However, in a circuit with a non-center tapped transformer, four diodes are required instead of the one needed for half-wave rectification.. Four diodes arranged this way are called a diode bridge or bridge rectifier.

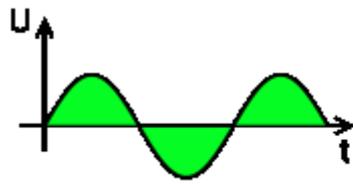

Input voltage

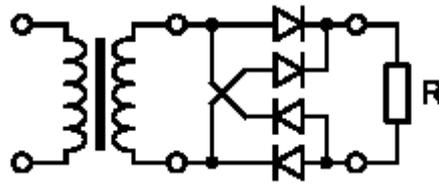


Full-wave rectifier

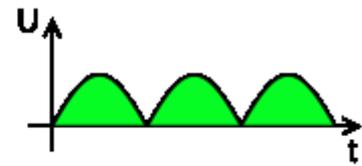


Output voltage

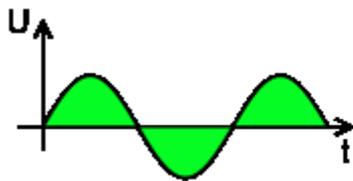
For single-phase AC, if the transformer is center-tapped, then two diodes back-to-back (i.e. anodes-to-anode or cathode-to-cathode) can form a full-wave rectifier. Twice as many windings are required on the transformer secondary to obtain the same output voltage compared to the bridge rectifier above.



Input voltage

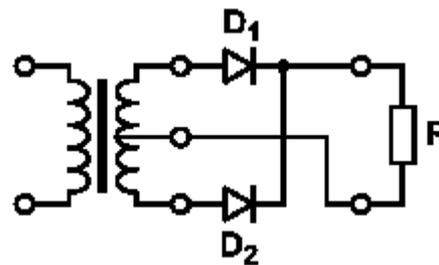

Full-wave rectifier

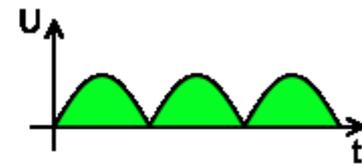

Output voltage

The average and root-mean-square output voltages of an ideal single phase full wave rectifier can be calculated as:

$$V_{rms} = \frac{V_p}{\sqrt{2}}$$


$$V_{dc} = V_{av} = \frac{2V_p}{\pi}$$

Equations

Where:

V_{dc}, V_{av} - the average or DC output voltage,
 V_p - the peak value of half wave,
 V_{rms} - the root-mean-square value of output voltage.

$\pi \approx 3.14159$

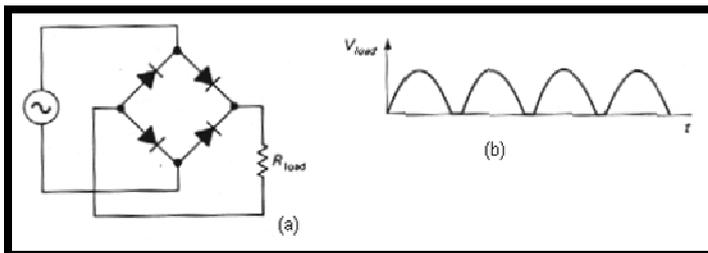

Full-way bridge rectifier with diode, using on the rectify both half-wave voltage sine wave. In the guidance of the bridged diodes are always two diodes conducting in the series.

Measurement:

1.) Measure the static transfer characteristic of half-wave rectifier.

In the **positive** direction:


Measurement no.	Input Voltage [V]	Output Voltage [V]
1	2	1,18
2	4	2,775
3	6	4,35
4	8	5,98
5	10	7,62
6	12	9,23
7	14	10,85
8	16	12,5
9	18	14,2
10	20	15,75

Table of measuring voltages

In the **negative** direction of voltage is always $U_{out} = 0$ V.

Measurement no.	Input voltage [V]	Output voltage [V]
1	-10	0
2	-8	0
3	-6	0
4	-4	0
5	-2	0


Table of measuring voltages

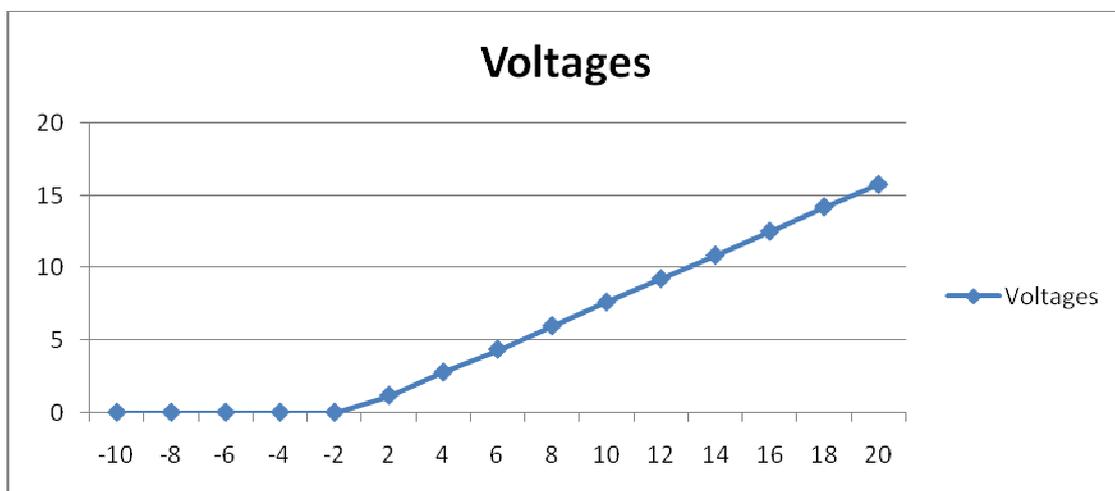

Graph of input/output voltages

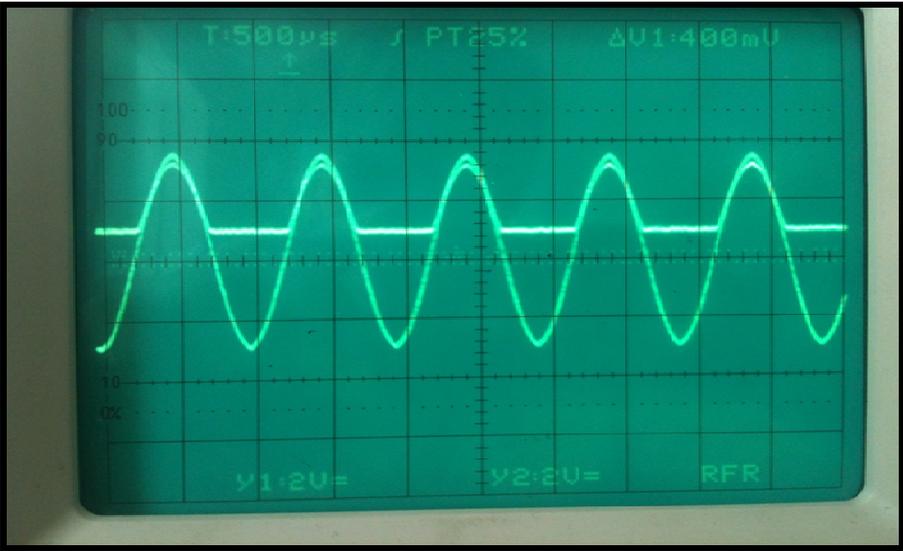2.) Measure the output waveform of half- wave rectifier in time domain with (and without) capacitor C, for different parameters of input periodic signal (frequency)


Without capacitors, the input and output waveforms weren't different by changing frequencies.




Picture no.1 – without capacitors

With big and small capacitors with different frequencies (Note: $100K \Rightarrow f=100 \text{ Hz}$):

f= x10

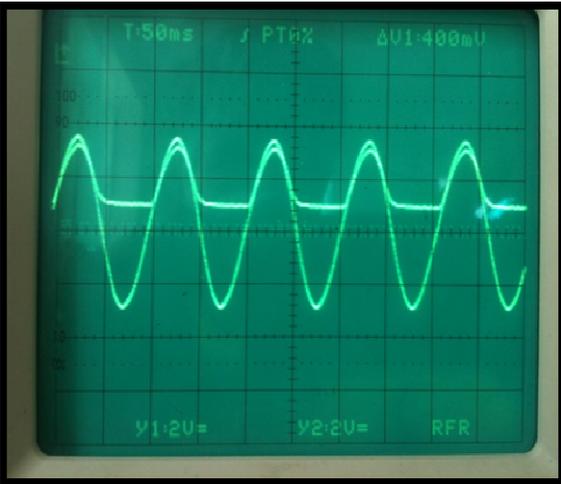


Picture no.2 – small capacitor

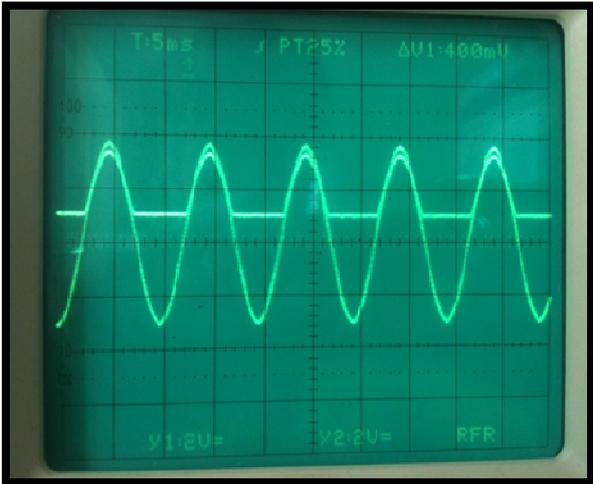


Picture no.3 – big capacitor

f= x100

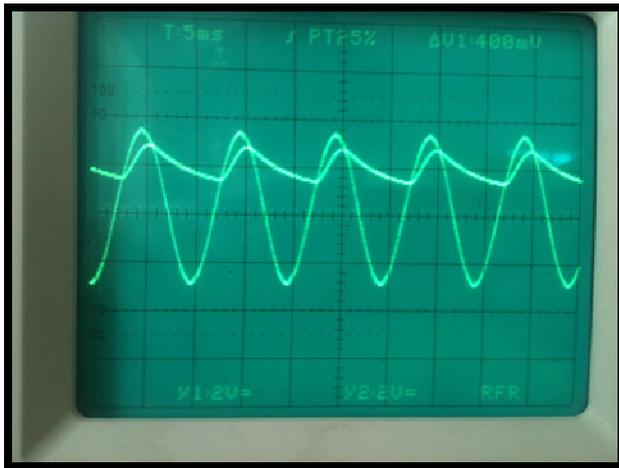


Picture no.4 – small capacitor

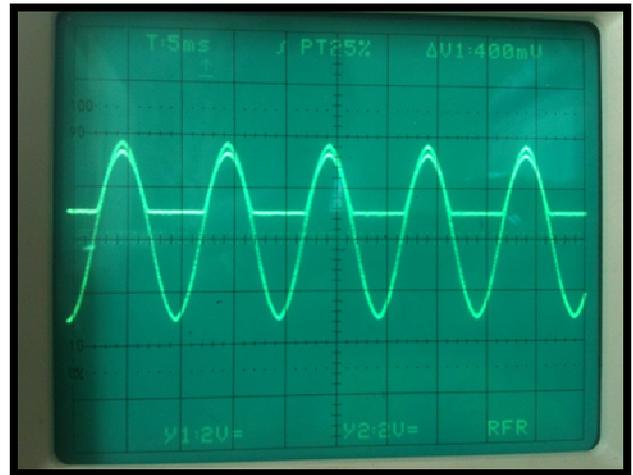


Picture no.5 – big capacitor

f= x10k

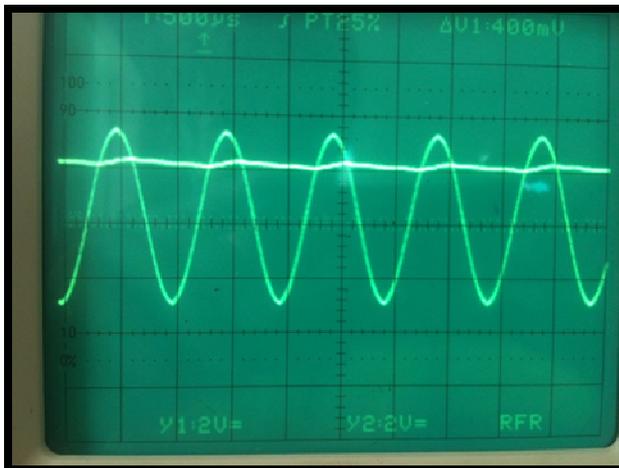


Picture no.6 – small capacitor

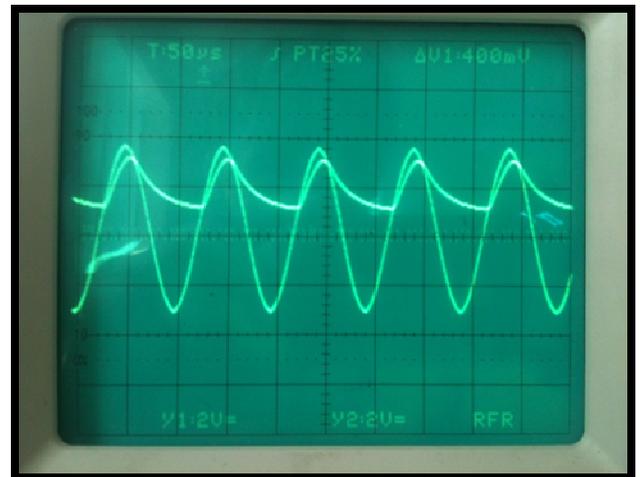


Picture no.7 – big capacitor

f= x100k

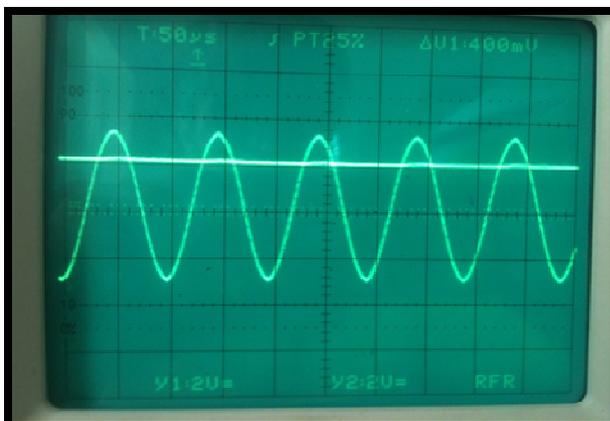


Picture no.8 – small capacitor

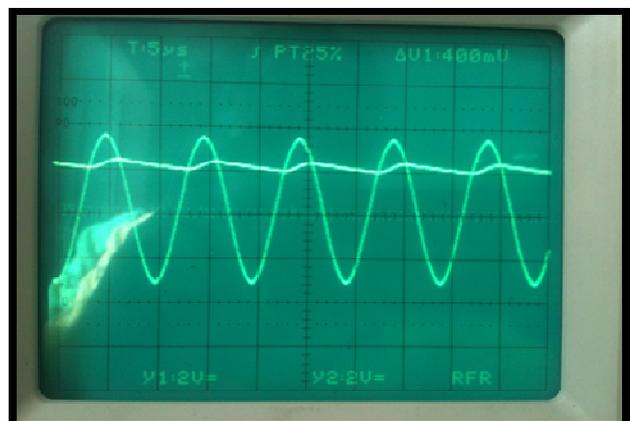


Picture no.9 – big capacitor

SPICE Simulations

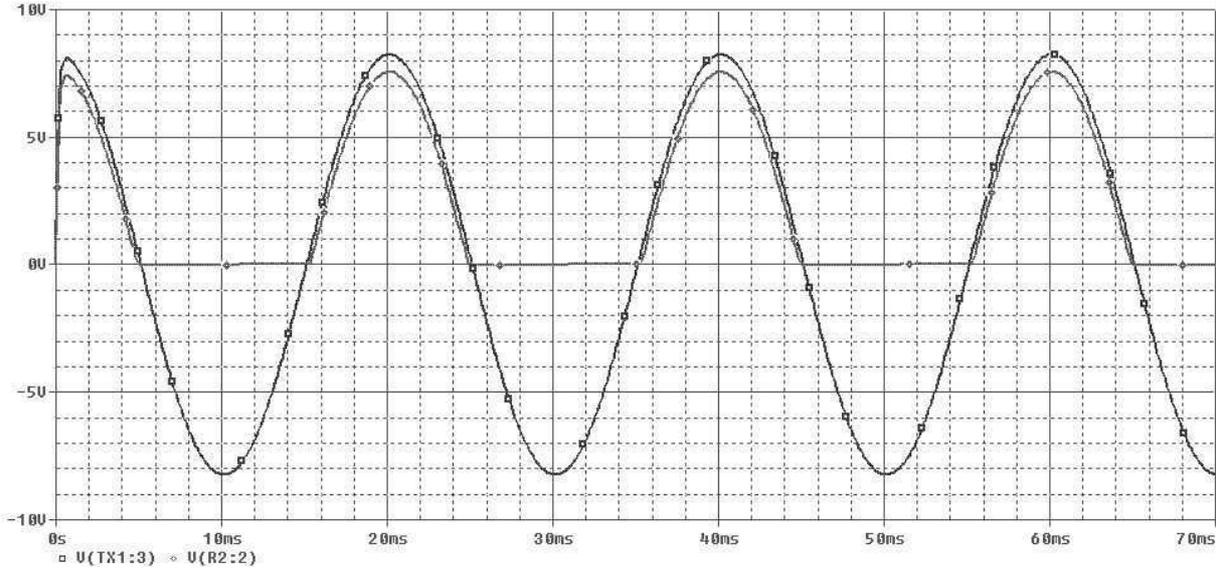
We have made a SPICE simulation according to the measurements and values given as output values. We changed the frequency and capacity, and we can see how the output changed on the pictures, taken from spice simulation.



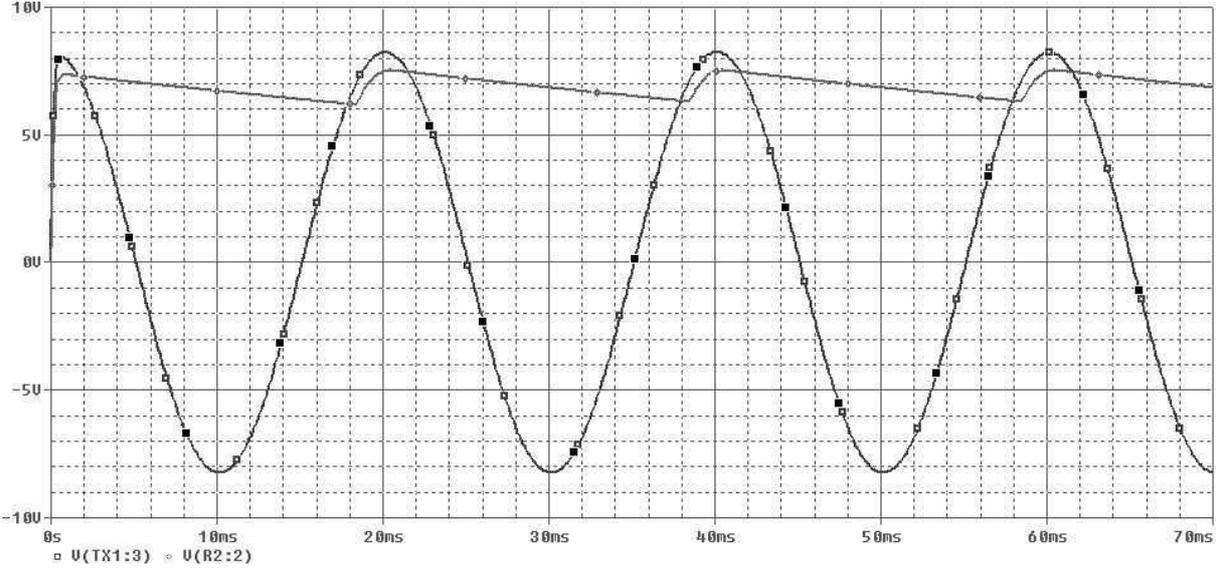Spice simulation no.1 – without capacitor, frequency did not changed the output lines



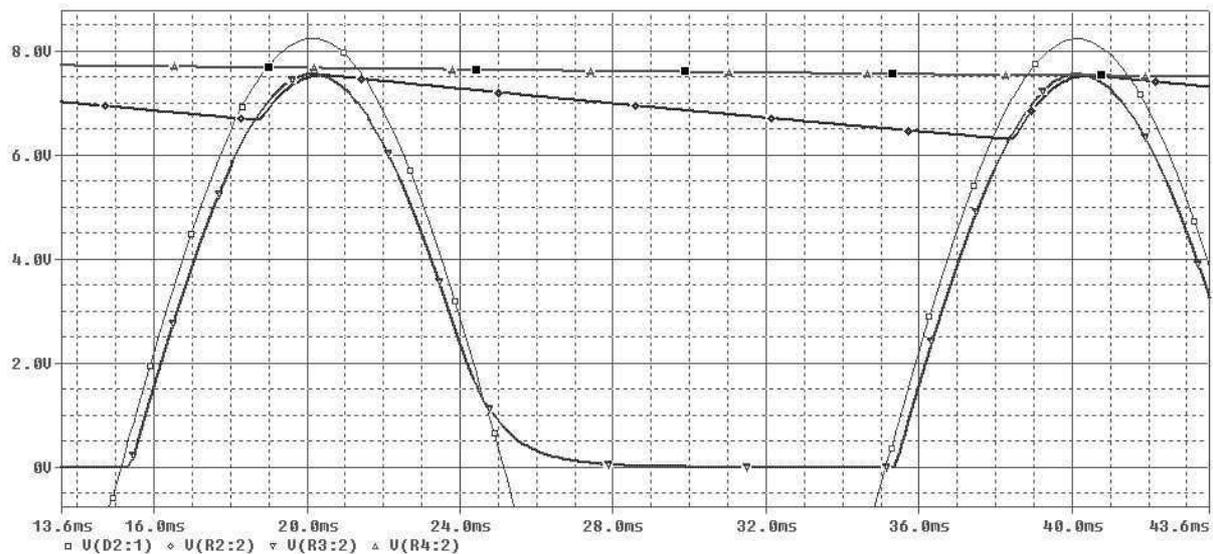Spice simulation no.2 – we used small capacitor, but higher frequency



Spice simulation no.3 – higher frequency changed the output line

Conclusion:

At the beginning of measurement, we have prepared voltmeter, oscilloscope, cables, multimeter and half-wave rectifier with 2 different capacitors. Then we've connected the circuit according to the figure on the picture. After that, we've connected the circuit to the oscilloscope and multimeter. We changed the frequency and by this changing, we have also changed amplitude and we were looking for a point where the output amplitude change almost into a straight line. That we applied in all three cases, without capacitor, with bigger and with smaller capacitor. Then we've connected circuit without capacitors into the multimeter and voltmeter and we we're changing input voltage and measuring the output voltage on the voltmeter.

We were trying to measure the most accurate, but for short time and our not very good skills, we weren't able to measure a more precisely results.

Resources:

http://en.wikipedia.org/wiki/Rectifier#Half-wave_rectification

<http://www.dnp.fmph.uniba.sk/~kollar/jewww/dioda.htm>

<http://alzat.szm.com/zdroje/jednocestny/jcusmsr.htmh>

<http://alzat.szm.com/zdroje/dvojcestny/dcusmsr.html>